

# Approximate Multiplication and Squaring Circuits with Parallel Correction

Patricio Bulić<sup>1</sup>, Jason Newman<sup>2</sup>

<sup>1</sup>Faculty of Computer and Information Science  
University of Ljubljana

<sup>2</sup>Faculty of Electrical Engineering  
University of Suburbia



# Agenda

- ▶ Motivation
- ▶ Approximate Multiplier and Squarer
- ▶ Hardware Implementation
- ▶ Error Analysis
- ▶ Conclusions

# Introduction

- ▶ Implementation bla bla:
  - ▶ bla bla bla
  - ▶ higher performance at smaller power consumption

# Introduction

- ▶ Implementation bla bla:
  - ▶ bla bla bla
  - ▶ higher performance at smaller power consumption
- ▶ Some beautiful chips:
  - ▶ noise and learning ability of analogue and digital designs
  - ▶ ASIC and FPGA (field programmable gate array)

# Introduction

- ▶ Implementation bla bla:
  - ▶ bla bla bla
  - ▶ higher performance at smaller power consumption
- ▶ Some beautiful chips:
  - ▶ noise and learning ability of analogue and digital designs
  - ▶ ASIC and FPGA (field programmable gate array)
- ▶ Signal processing applications incorporate complex algorithms with many multiplications
  - ▶ Multiplication is area, power and time consuming operation
  - ▶ bla bla bla

# Approximate Multiplier

- ▶ An approximate multiplier, introduced by Babic et al. (2010):
  - ▶ Reduced usage of logic resources: one adder and a shifter
  - ▶ Reduced power consumption
- ▶ The product of the two numbers,  $N_1$  and  $N_2$

$$N_1 \cdot N_2 = (2^{k_1} + N_1^{(1)}) \cdot (2^{k_2} + N_2^{(1)})$$

# Approximate Multiplier

- ▶ An approximate multiplier, introduced by Babic et al. (2010):
  - ▶ Reduced usage of logic resources: one adder and a shifter
  - ▶ Reduced power consumption
- ▶ The product of the two numbers,  $N_1$  and  $N_2$

$$\begin{aligned} N_1 \cdot N_2 &= (2^{k_1} + N_1^{(1)}) \cdot (2^{k_2} + N_2^{(1)}) \\ &= 2^{k_1+k_2} \end{aligned}$$

1. shift left the leading "1" from the first number by  $k_2$  places

# Approximate Multiplier

- ▶ An approximate multiplier, introduced by Babic et al. (2010):
  - ▶ Reduced usage of logic resources: one adder and a shifter
  - ▶ Reduced power consumption
- ▶ The product of the two numbers,  $N_1$  and  $N_2$

$$\begin{aligned}N_1 \cdot N_2 &= (2^{k_1} + N_1^{(1)}) \cdot (2^{k_2} + N_2^{(1)}) \\&= 2^{k_1+k_2} + N_1^{(1)} \cdot 2^{k_2}\end{aligned}$$

1. shift left the leading "1" from the first number by  $k_2$  places
2. shift left the first remainder by  $k_2$  places



# Approximate Multiplier

- ▶ An approximate multiplier, introduced by Babic et al. (2010):
  - ▶ Reduced usage of logic resources: one adder and a shifter
  - ▶ Reduced power consumption
- ▶ The product of the two numbers,  $N_1$  and  $N_2$

$$\begin{aligned}N_1 \cdot N_2 &= (2^{k_1} + N_1^{(1)}) \cdot (2^{k_2} + N_2^{(1)}) \\&= 2^{k_1+k_2} + N_1^{(1)} \cdot 2^{k_2} + N_2^{(1)} \cdot 2^{k_1}\end{aligned}$$

1. shift left the leading "1" from the first number by  $k_2$  places
2. shift left the first remainder by  $k_2$  places
3. shift left the second remainder by  $k_1$  places

# Approximate Multiplier

- ▶ An approximate multiplier, introduced by Babic et al. (2010):
  - ▶ Reduced usage of logic resources: one adder and a shifter
  - ▶ Reduced power consumption
- ▶ The product of the two numbers,  $N_1$  and  $N_2$

$$\begin{aligned}N_1 \cdot N_2 &= (2^{k_1} + N_1^{(1)}) \cdot (2^{k_2} + N_2^{(1)}) \\&= 2^{k_1+k_2} + N_1^{(1)} \cdot 2^{k_2} + N_2^{(1)} \cdot 2^{k_1} + N_1^{(1)} \cdot N_2^{(1)}\end{aligned}$$

1. shift left the leading "1" from the first number by  $k_2$  places
2. shift left the first remainder by  $k_2$  places
3. shift left the second remainder by  $k_1$  places
4. multiply the two remainders

# Approximate Multiplier

- ▶ An approximate multiplier, introduced by Babic et al. (2010):
  - ▶ Reduced usage of logic resources: one adder and a shifter
  - ▶ Reduced power consumption
- ▶ The product of the two numbers,  $N_1$  and  $N_2$


$$\begin{aligned} N_1 \cdot N_2 &= (2^{k_1} + N_1^{(1)}) \cdot (2^{k_2} + N_2^{(1)}) \\ &= 2^{k_1+k_2} + N_1^{(1)} \cdot 2^{k_2} + N_2^{(1)} \cdot 2^{k_1} + N_1^{(1)} \cdot N_2^{(1)} \end{aligned}$$

1. shift left the leading "1" from the first number by  $k_2$  places
2. shift left the first remainder by  $k_2$  places
3. shift left the second remainder by  $k_1$  places
4. multiply the two remainders

# Hardware Implementation

- A Basic block implements the approximate product


$$(N_1 \cdot N_2)_{approx} =$$

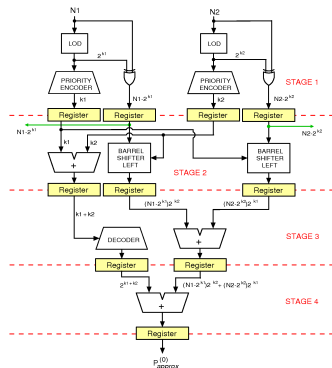
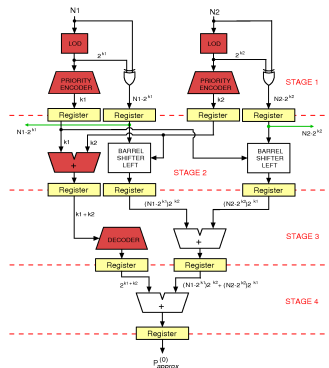
# Hardware Implementation

- A Basic block implements the approximate product


$$(N_1 \cdot N_2)_{approx} = 2^{k_1+k_2}$$


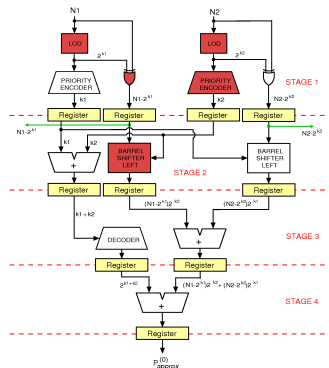
# Hardware Implementation

- A Basic block implements the approximate product


$$(N_1 \cdot N_2)_{approx} = 2^{k_1+k_2} N_1^{(1)} \cdot 2^{k_2}$$


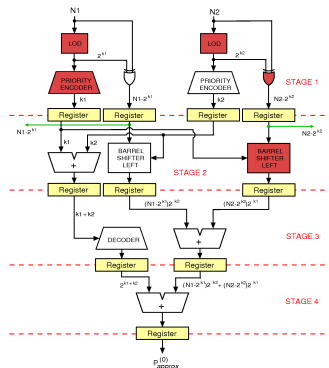
# Hardware Implementation

- A Basic block implements the approximate product


$$(N_1 \cdot N_2)_{approx} = 2^{k_1+k_2} \\ N_1^{(1)} \cdot 2^{k_2} \\ N_2^{(1)} \cdot 2^{k_1}$$


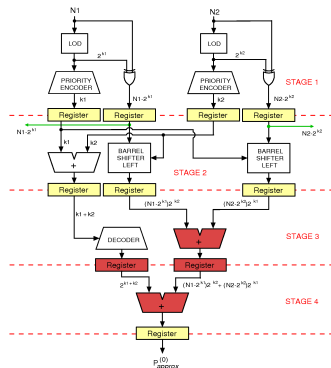
# Hardware Implementation

- A Basic block implements the approximate product

$$\begin{aligned}
 (N_1 \cdot N_2)_{approx} &= 2^{k_1+k_2} \\
 &+ N_1^{(1)} \cdot 2^{k_2} \\
 &+ N_2^{(1)} \cdot 2^{k_1}
 \end{aligned}$$





# Error Analysis

## Theorem

*The probability of an error in the circuit is directly proportional to the trouble it can cause.*

# Error Analysis

## Theorem





*The probability of an error in the circuit is directly proportional to the trouble it can cause.*

## Proof.

The proof is straightforward.



# Errors

    

# Conclusions

- ▶ The proposed approach improves the average and maximum relative errors compared to the existing square approximations.

# Conclusions

- ▶ The proposed approach improves the average and maximum relative errors compared to the existing square approximations.
- ▶ Error analysis has shown that an error in the circuit is directly proportional to the trouble it can cause.

# Conclusions

- ▶ The proposed approach improves the average and maximum relative errors compared to the existing square approximations.
- ▶ Error analysis has shown that an error in the circuit is directly proportional to the trouble it can cause.
- ▶ We can calculate the correction terms in parallel.